

Ojus Anand

M12258703

ECE 2060 / Lab 3

Sept. 17, 2017

Report Due:

Sept. 18, 2017

Computer Interface Design: Project Design Report

Requirements:

- Summary: Simulating the computer interface to a design printer, seven inputs must indicate the printing of a character, a return, and a movement to the line's beginning.

• Inputs: A - G

• Outputs: X, Y, Z

- X will only output logic 1 for the command to go to a line's beginning (13_{10})

- Y will only output logic 1 when the command for a newline is given (10_{10})

- Z will only output logic 1 for a printable character $32_{10} - 127_{10}$

- A - G will be switches while X, Y, Z will be LEDs in this lab

- Due to the massive amounts of inputs, a truth table should be avoided

Design:


• Boolean Expression:

- $Z = A + B$

- $X = (DEG)(Z + C + F)'$

- $Y = (DF)(Z + C + E + G)'$

• Gate Design:

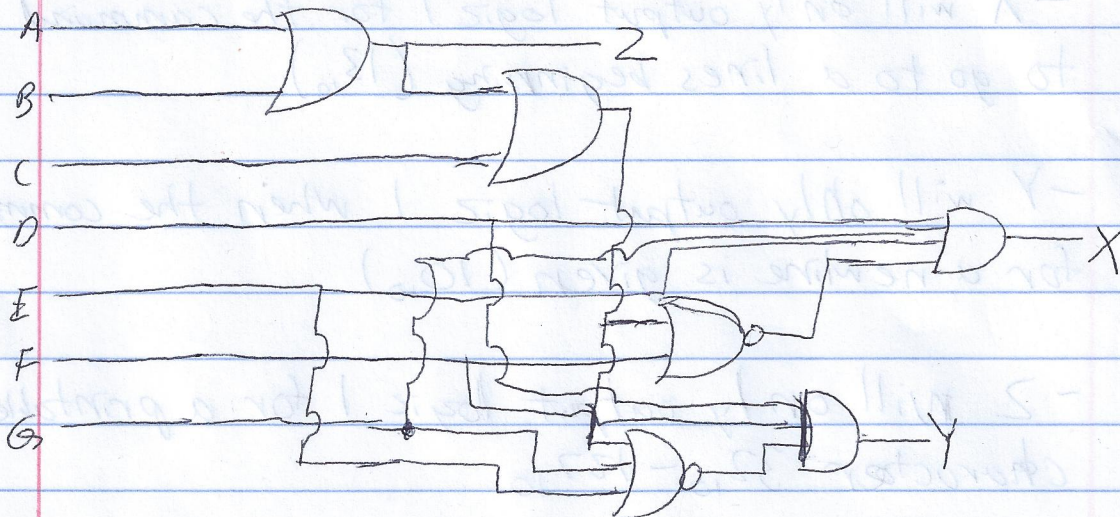

Test Procedure:

A	B	C	D	E	F	G	X	Y	Z	Purpose
0	0	0	0	0	0	0	0	0	0	How does it work with nothing
0	0	0	1	1	0	1	1	0	0	Does X work and others not
0	0	0	1	0	1	0	0	1	0	Does Y work and others don't
0	1	0	0	0	0	0	0	0	1	Does Z start
1	0	0	0	0	0	0	0	0	1	Testing Z
1	1	1	1	1	1	1	0	0	1	Z final test

Duration: 3 hrs