

Tire Pressure Indicator

Project Design Report

Start time: 6:00 PM

Requirements:

- Summary - Three inputs (A, B, and C) must generate three different outputs (L, M, H) based on inputs.

- Inputs: A, B, C

- Outputs: L, M, H

- Output Possibilities

- L is logic 1 (H and M are 0) when $ABC \leq 2$
(ie. $ABC = 000, 001, 010$)

- M generates logic 1 (L and H are 0) when $2 < ABC < 5$ (ie. $ABC = 011, 100$)

- H is logic 1 (L and M are 0) when $ABC > 4$ (ie. $ABC = 101, 110, 111$)

- A, B, C are switches while L, M, H are LEDs.

Design:

• Truth Table -

A	B	C	L	M	H
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	0	0	1
1	1	1	0	0	1

• Boolean Expressions -

$$- A'B'C' + A'B'C + A'BC' = L$$

$$A'(B'C' + B'C + BC') = L$$

$$A' [B'(C' + C) + BC'] = L$$

$$A'(B' + BC') = L$$

$$A'(B' + C') = L$$

$$- AB'C + ABC' + ABC = H$$

$$AC(B' + B) + ABC' = H$$


$$AC + ABC' = H$$

$$A(C + C'B) = H$$

$$A(C + B) = H$$

$$-M = (L + H)'$$

• Grate Design =

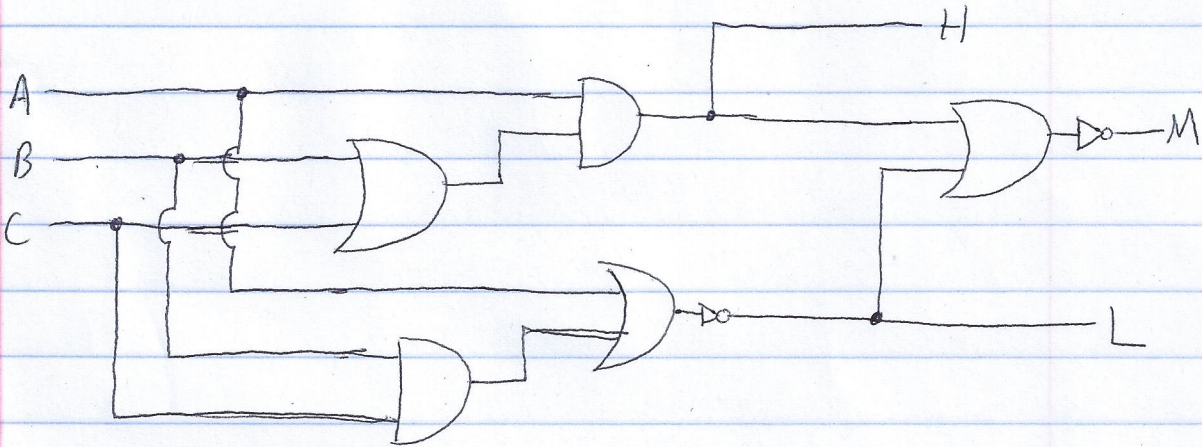

• Test Procedure:

Test #	A	B	C	Expected			Actual		
				L	M	H	L	M	H
1	0	0	0	1	0	0			
2	0	0	1	1	0	0			
3	0	0	0	1	0	0			
4	0	1	1	0	1	0			
5	1	0	0	0	0	0			
6	1	0	1	0	0	1			
7	1	1	0	0	0	1			
8	1	1	1	0	0	1			

End Time: 7:21 km

Total Duration: 1 hr 21 min