


Lab 7: Sequence Detector Implementation using a Breadboard

Requirements:

- Design a synchronous sequential circuit to recognize a sequence of at least a single logic 1 followed by a logic 0
- Sequential Circuit must be a Moore machine and can use three states: S0, S1, and S2
- Two D-FFs will be utilized and an S3 state is optional for utilizing “don’t cares”
- Input I can be implemented via a switch whilst output Z can be implemented by an LED
- It is recommended to utilize a push-button rather than a clock generator for a 1 Hz clock signal
- Implement an active-low preset option and an active-low clear option. Make sure to set them both to logic 1 after setting clear to 0 for state initialization

Design

- State Diagram

 

- State Table

Present State	Input (I)	Next State	Output (Z)
S ₀	0	S ₀	0
	1	S ₁	0
S ₁	0	S ₂	0
	1	S ₁	0
S ₂	0	S ₀	1
	1	S ₁	1
S ₃	0	D	D
	1	D	D

- State Assignment

Present State <u>A</u> <u>B</u>	Input (I)	Next State <u>A</u> <u>B</u>	Output (Z)
0 0	0	0 0	0
	1	0 1	0
0 1	0	1 0	0
	1	0 1	0
1 0	0	0 0	1
	1	0 1	1
1 1	0	D D	D
	1	D D	D

- FF-type selection
 - Two D flip-flops to represent three states with outputs A and B. There is a single input, “I”, and a single output, “Z”:
 - $A(t + 1) = D_A(A, B, I) = \Sigma(2)$
 - $B(t + 1) = D_B(A, B, I) = \Sigma(1, 3, 5)$
 - $Z(A, B, I) = \Sigma(4, 5)$
- Simplified FF input equations and output equations

- D_A :

BI					
A		00	01	11	10
0					1
1				D	D

$$D_A = BI'$$

- D_B :

BI					
A		00	01	11	10
0			1	1	
1			1	D	D


$$D_B = I$$

- Z:

BI					
A		00	01	11	10
0					
1		1	1	D	D

$$Z = A$$

- Logic Diagram

 

Testing

- Test Patterns:

Input I	CLR	PR	Output Z
00000	1	1	00000
11111	1	1	00000
01100101001	1	1	00010010100
11101	0	1	00000

01001	1	0	11111
10110	0	0	00000

- Simulation:

- Verilog D_FF:

```
module D_FF(Q, D, CLK, Clr);
    output Q;
    input D, CLK, Clr;
    reg Q;

    always @(posedge CLK, negedge Clr)
        if (~Clr) Q <= 1'b0; else Q <= D;
endmodule
```

- Verilog Sequential Circuit:

```
module Moore_sequential(output Z, A, B,
    input I, clock, reset
);
    wire Da, Db;

    assign Da = B&&(~I);
    assign Db = I;
    assign Z = A;

    D_FF m1(A, Da, clock, reset);
    D_FF m2(B, Db, clock, reset);
endmodule
```

- Verilog Testbench:

```

module Sim;
    // Inputs
    reg I;
    reg clock;
    reg reset;

    // Outputs
    wire Z;
    wire A;
    wire B;

    // Instantiate the Unit Under Test (UUT)
    Moore_sequential uut (
        .Z(Z),
        .A(A),
        .B(B),
        .I(I),
        .clock(clock),
        .reset(reset)
    );

    // Initialize Inputs
    initial begin
        I = 0;
        clock = 0;
        reset = 1;
        #2 reset = 0;
        #2 reset = 1;

        repeat (22)
            #5 clock = ~ clock; //used to generate 15 clock cycles
        end

        // Add stimulus here
        initial begin
            #10 I = 1; //Change the input patterns to fully simulate your circuit
            #20 I = 0;
            #20 I = 1;
            #10 I = 0;
            #10 I = 1;
            #10 I = 0;
            #20 I = 1;
            #10 I = 0;
        end
    end
endmodule

```

Design Time: 5 hr